

Name : _____

Electrical Circuits

Electrical Circuit	Description	Circuit
Open Circuit	An electric circuit in which the current flow is interrupted by a broken wire or an open switch.	
Closed Circuit	An electric circuit in which the current flows through an uninterrupted path.	
Series Circuit	An electric circuit in which the current flows through one path and a break in the circuit prevents the current flow.	
Parallel Circuit	An electric circuit in which the current flows through more than one path. A break in the circuit does not prevent the flow of the current.	