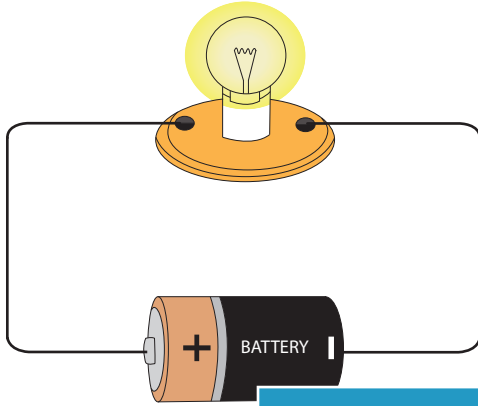


Name : _____


Open and Closed Circuits

Examine each electric circuit and write whether the bulb(s) 'will light' or 'will not light'.


1)



2)

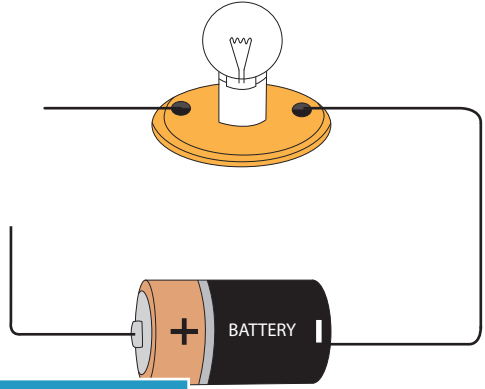

3)

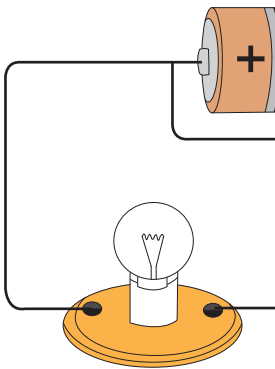

PREVIEW

Access the largest collection of worksheets for just **\$19.95** per year!


Members, please log in to download this worksheet.

Log in



Not a member? Please sign up to gain complete access.

Sign up

www.mathworksheets4kids.com

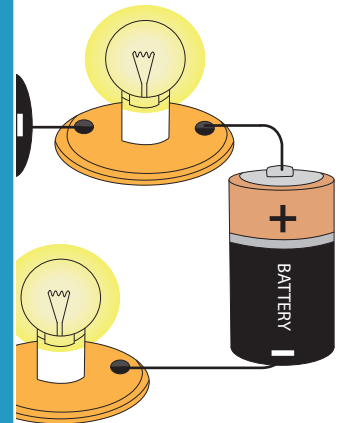


5)

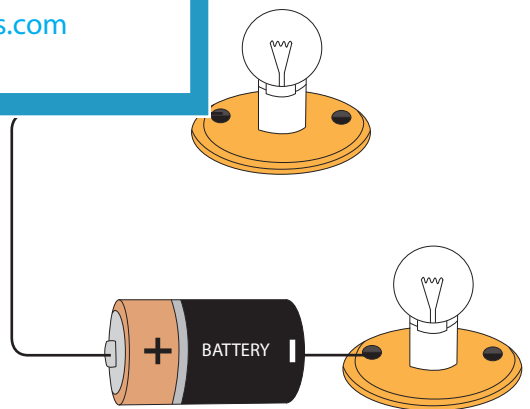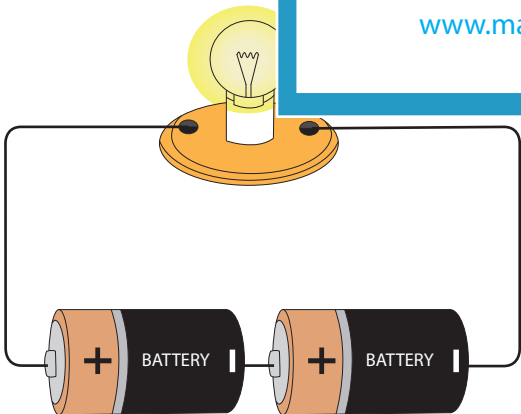

Open and Closed Circuits


Examine each electric circuit and write whether the bulb(s) 'will light' or 'will not light'.

1)

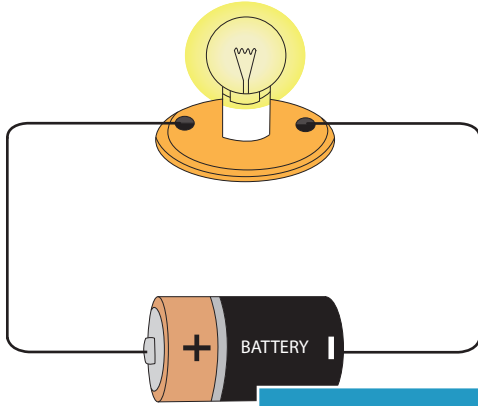


will light

2)

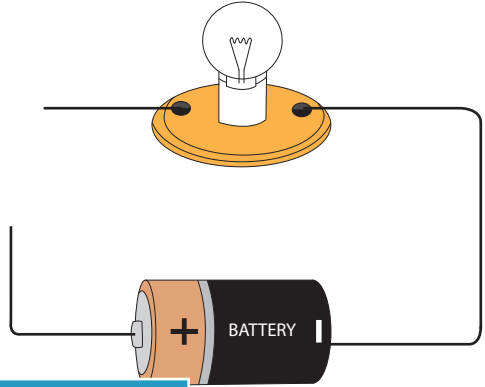

not light

3)

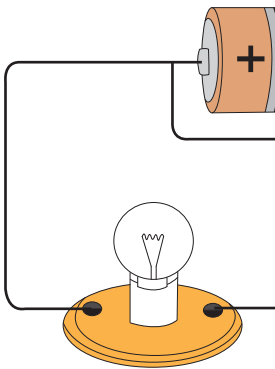

will not

Access the largest collection of worksheets for just **\$19.95** per year!


Members, please log in to download this worksheet.

Log in

Not a member? Please sign up to gain complete access.


Sign up

www.mathworksheets4kids.com

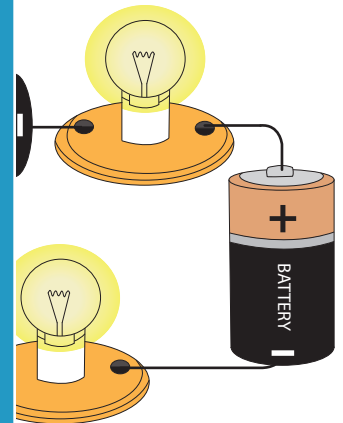


ll light

5)

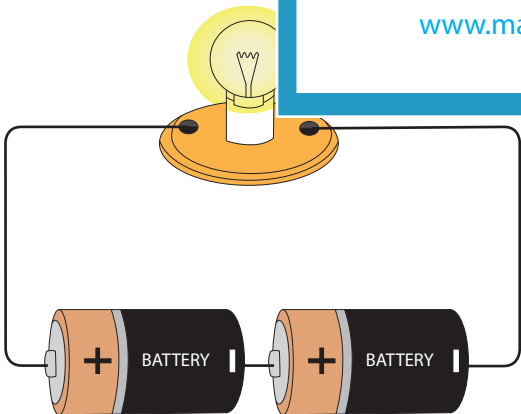

will light

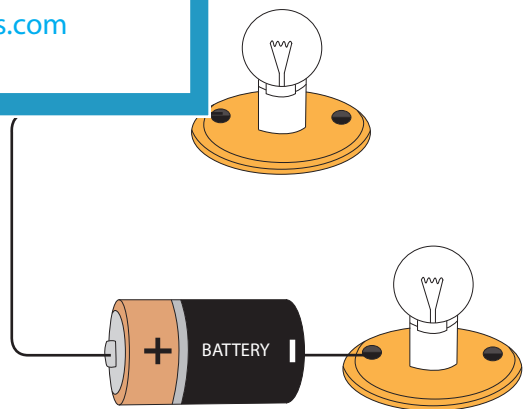

will not light