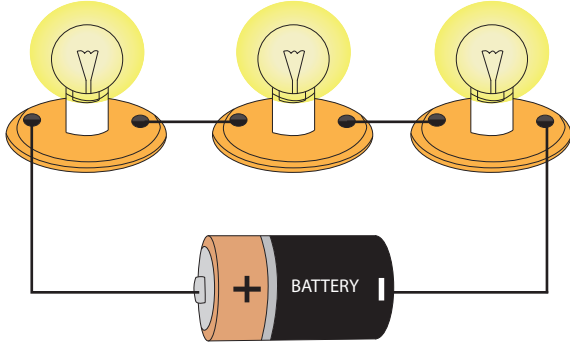


Name : _____


Series and Parallel Circuits

Examine each electric circuit. State whether it is series or parallel.



1)





2)

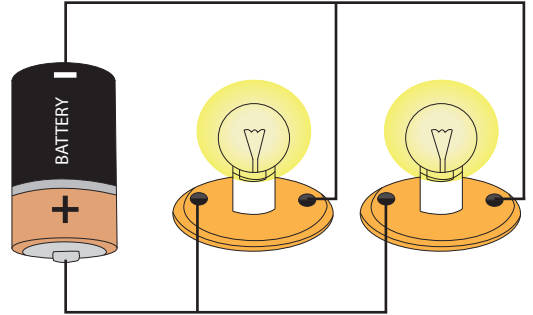

3)

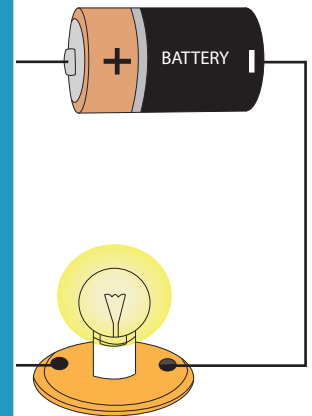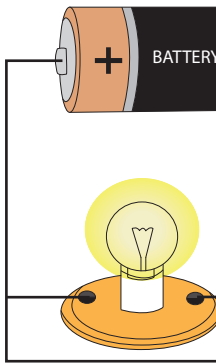

5)

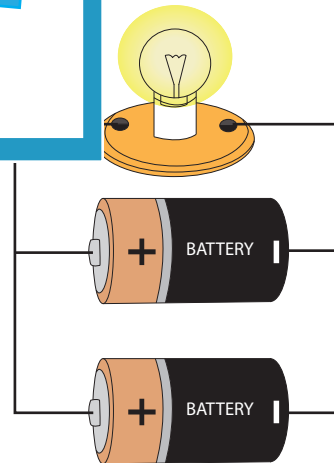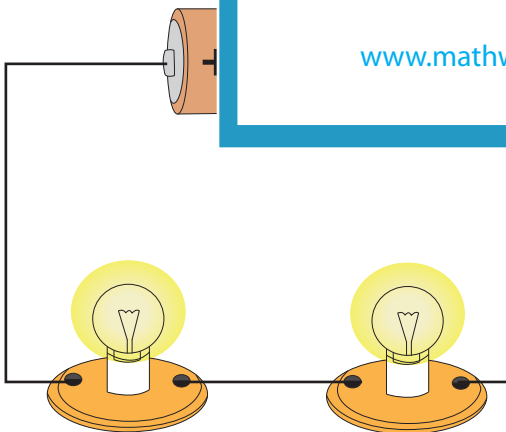

PREVIEW

Access the largest collection of worksheets for just **\$19.95** per year!

Members, please log in to download this worksheet.

Log in



Not a member? Please sign up to gain complete access.

Sign up

www.mathworksheets4kids.com



Series and Parallel Circuits

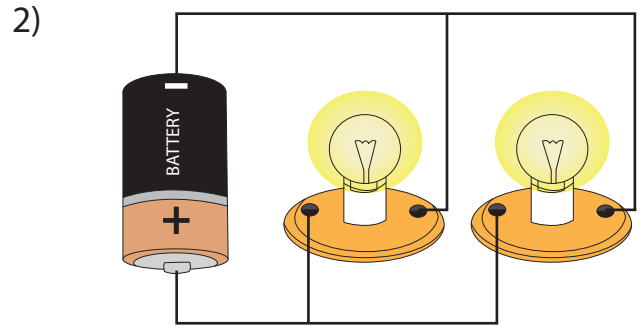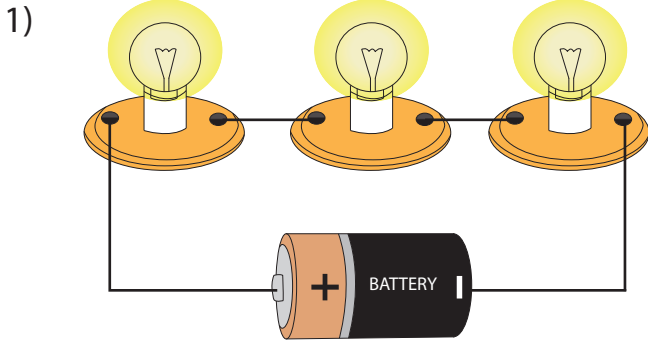Examine each electric circuit. State whether it is series or parallel.





series

parallel circuit

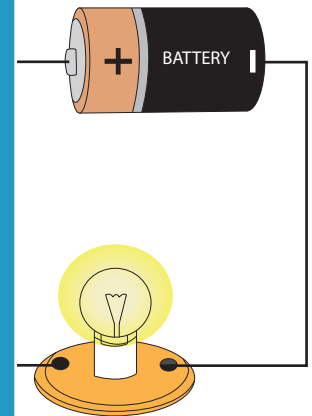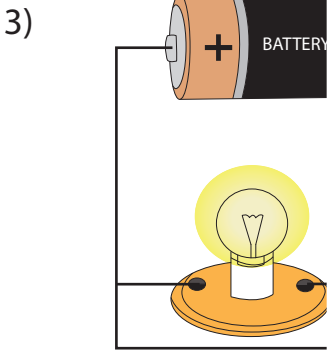

parallel

series circuit

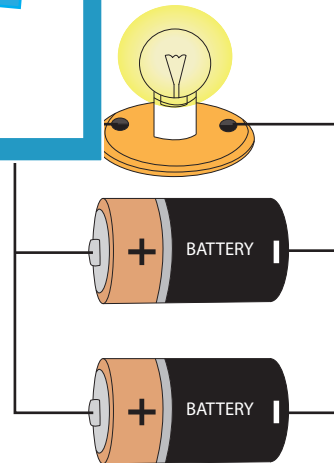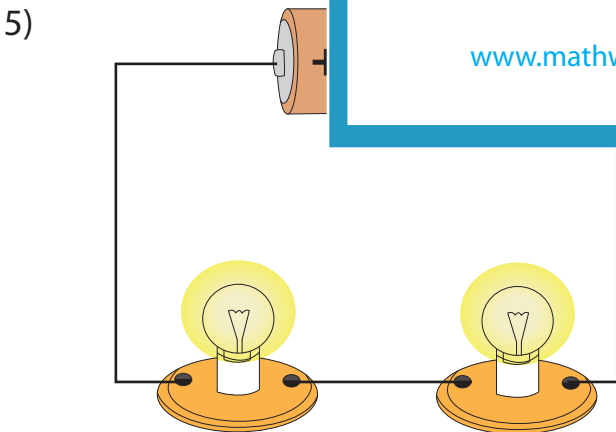

series circuit

parallel circuit

PREVIEW

Access the largest collection of worksheets for just **\$19.95** per year!

Members, please log in to download this worksheet.

Not a member? Please sign up to gain complete access.

www.mathworksheets4kids.com

Log in **Sign up**